




Ejemplos del capítulo 3

Circuitos eléctricos I



PRACTICE

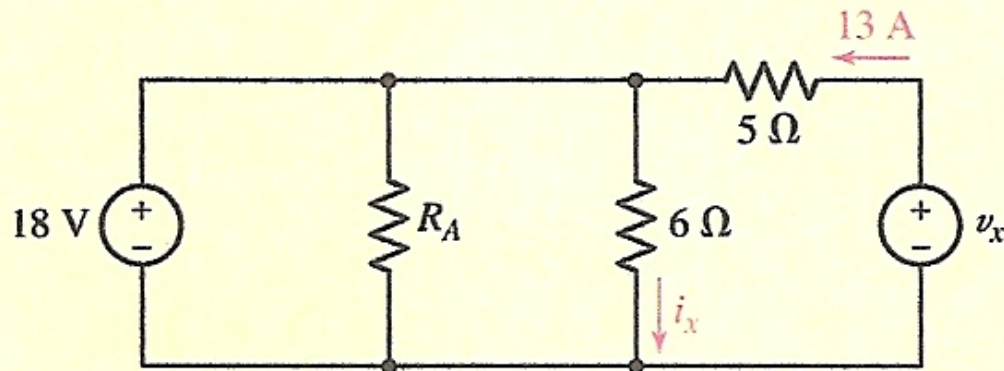3.1 Count the number of branches and nodes in the circuit in Fig. 3.4. If $i_x = 3$ A and the 18 V source delivers 8 A of current, what is the value of R_A ? (Hint: You need Ohm's law as well as KCL.)



■ FIGURE 3.4

Ans: 5 branches, 3 nodes, 1Ω.



Problema 3.2 página 63

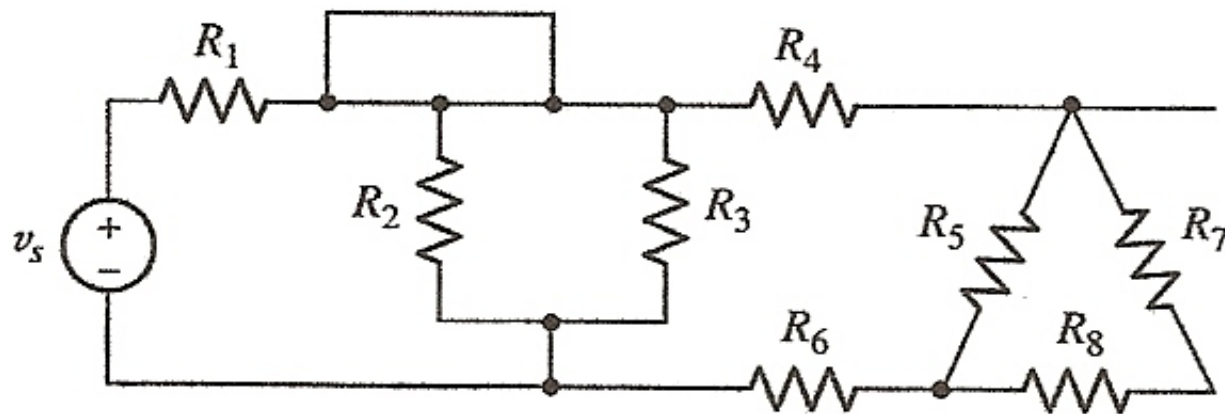



FIGURE 3.42

2. In the circuit of Fig. 3.42, count the number of (a) nodes; (b) branches.



Problema 3.6 página 64

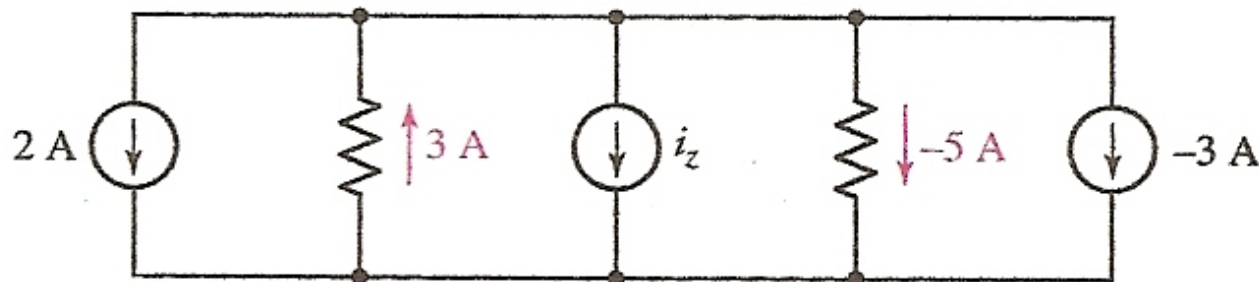6. (a) Determine the current labeled i_z in the circuit shown in Fig. 3.45. (b) If the resistor carrying 3 A has a value of $1\ \Omega$, what is the value of the resistor carrying -5 A ?




■ **FIGURE 3.45**



Problema 3.8 página 64

8. Referring to Fig. 3.47,

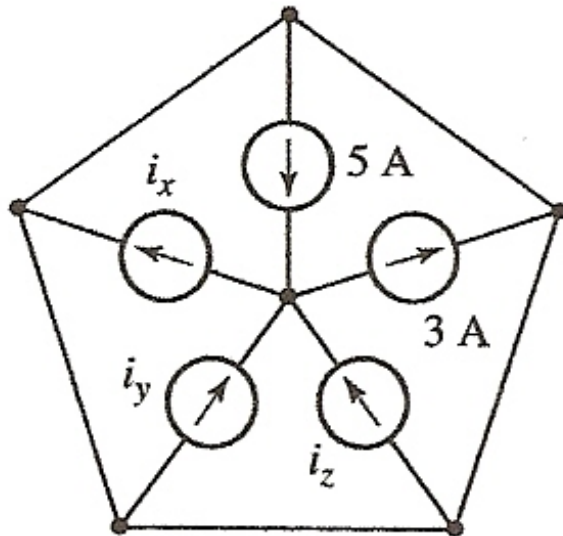- (a) Find i_x if $i_y = 2 \text{ A}$ and $i_z = 0 \text{ A}$. (b) Find i_y if $i_x = 2 \text{ A}$ and $i_z = 2 i_y$.
(c) Find i_z if $i_x = i_y = i_z$.




■ FIGURE 3.47



Problema 3.9 página 64

9. Find i_x and i_y in the circuit of Fig. 3.48.

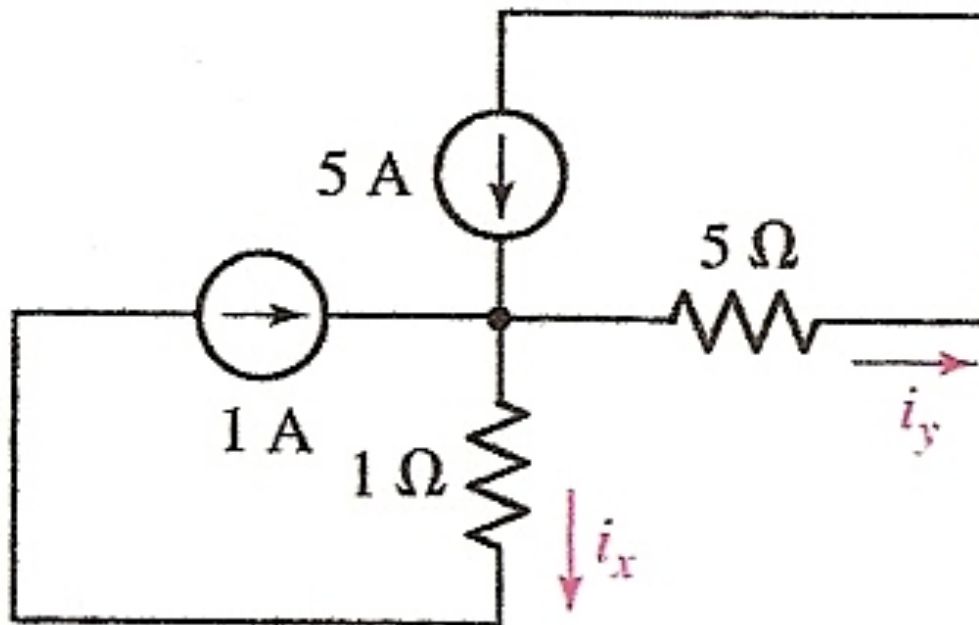




Problema 3.13 página 65

13. In the circuit of Fig. 3.50,

(a) Calculate v_y if $i_z = -3$ A.

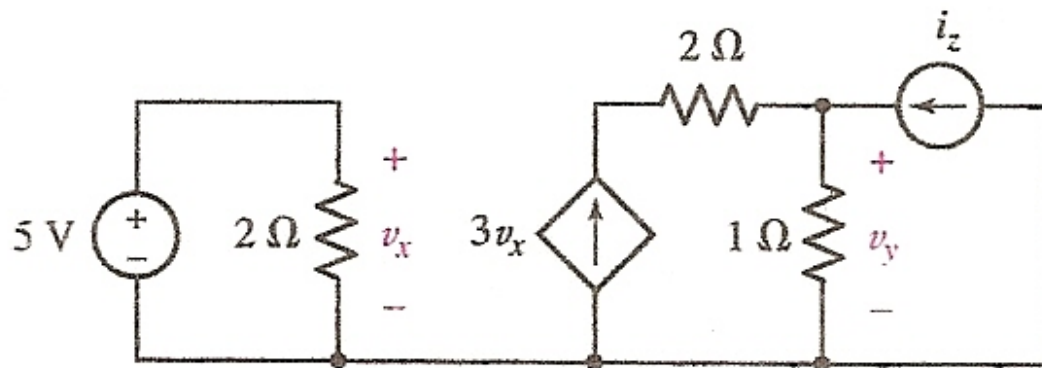(b) What voltage would need to replace the 5 V source to obtain $v_y = -6$ V if $i_z = 0.5$ A?




Circuitos eléctricos I
FIGURE 3.50

Dr. Javier Cuevas




Problema 3.15 página 65

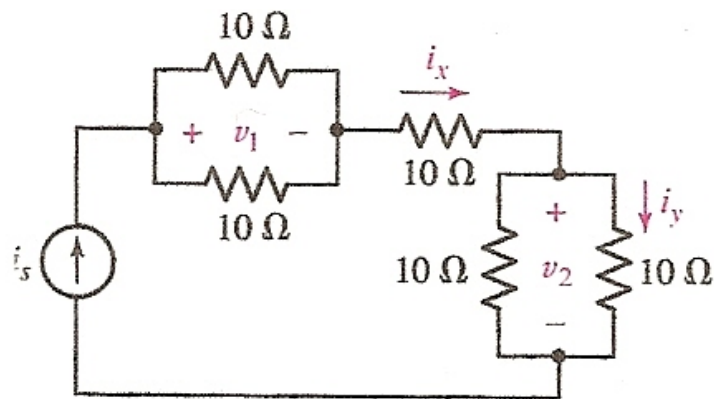15. Find R and G in the circuit of Fig. 3.51b if the 5 A source is supplying 100 W and the 40 V source is supplying 500 W.



(a)

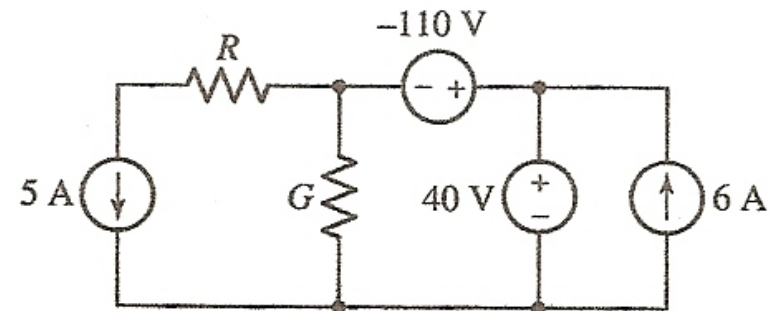

(b)

■ FIGURE 3.51



Problema 3.16 página 66

16. In the circuits of Fig. 3.52a and b, determine the current labeled i .



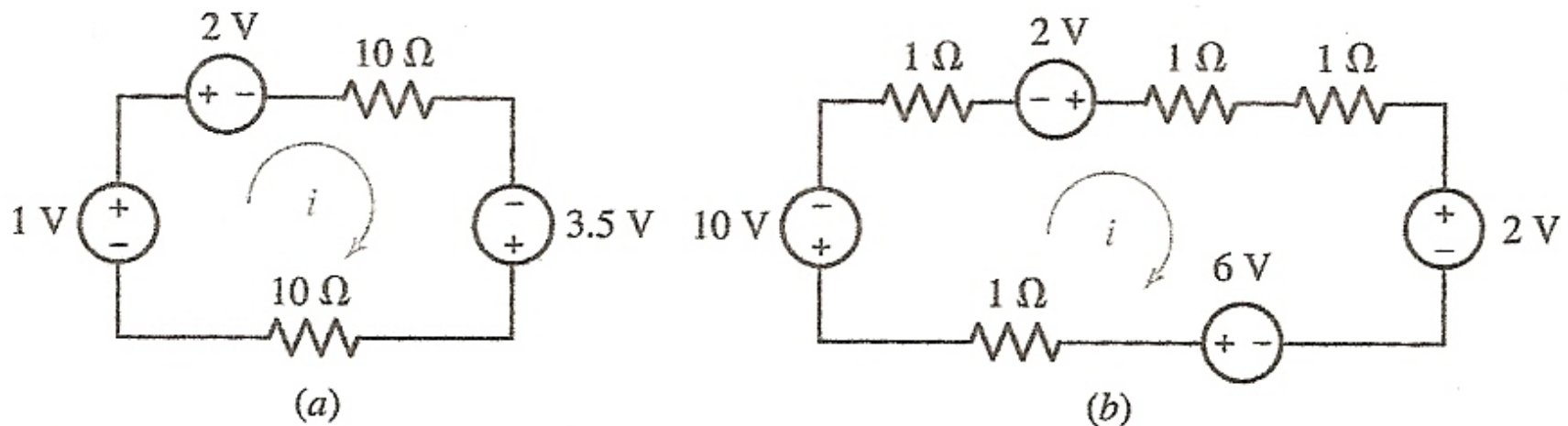


FIGURE 3.52

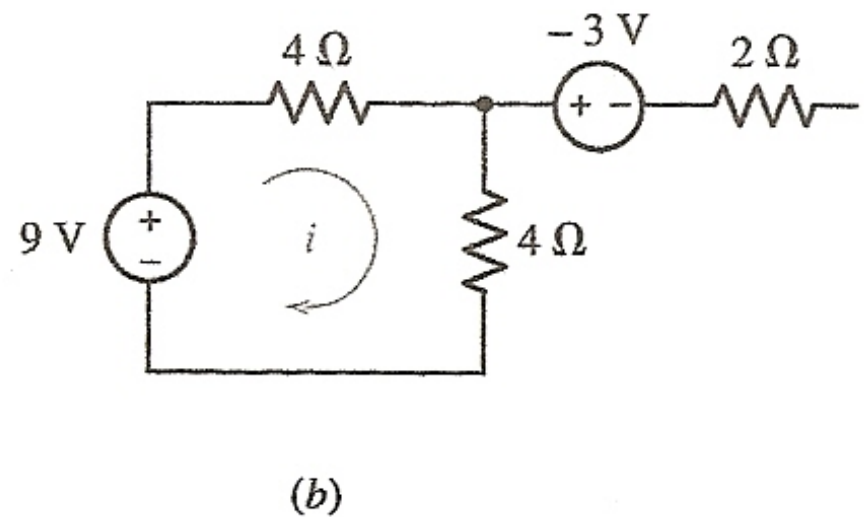

Problema 3.17 página 66

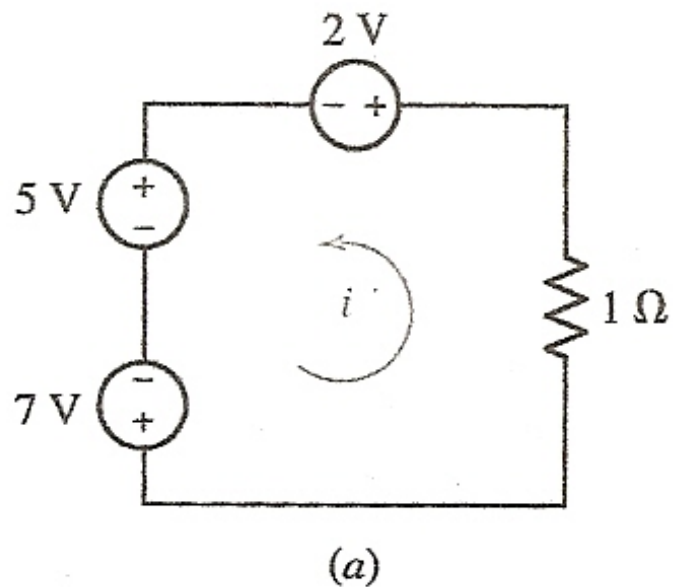17. Calculate the value of i in each circuit of Fig. 3.53.




■ **FIGURE 3.53**



Problema 3.18 página 66

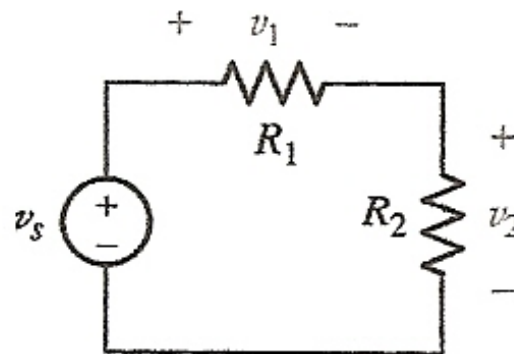18. Consider the simple circuit shown in Fig. 3.54. Using KVL, derive the expressions

$$v_1 = v_s \frac{R_1}{R_1 + R_2} \quad \text{and} \quad v_2 = v_s \frac{R_2}{R_1 + R_2}$$




■ **FIGURE 3.54**



Problema 3.30 página 68

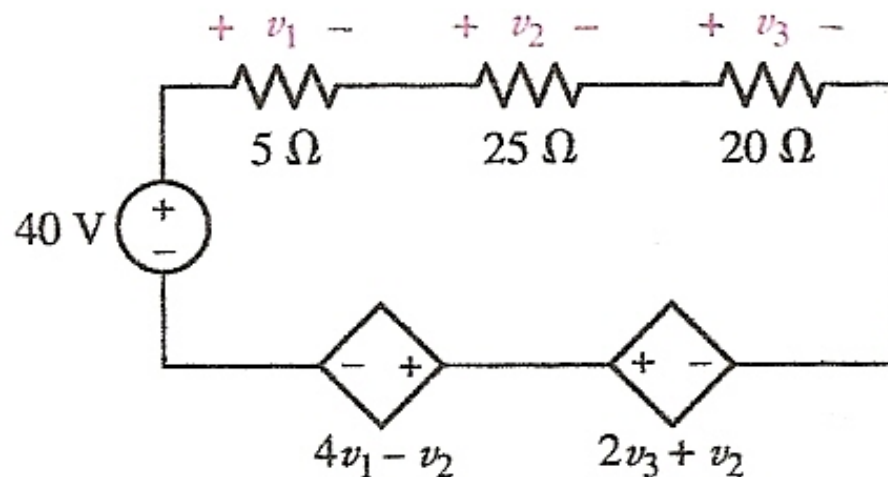30. Find the power absorbed by each of the six circuit elements in Fig. 3.63, and show that they sum to zero.




■ **FIGURE 3.63**



Problema 3.35 página 69

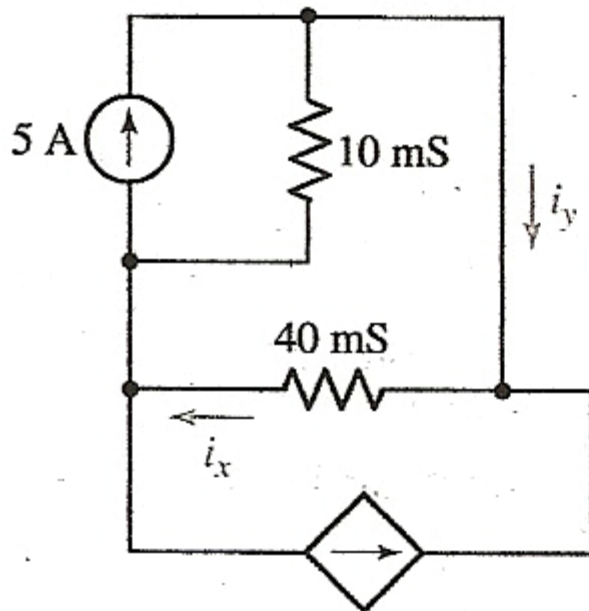35. Find the power absorbed by each circuit element of Fig. 3.68 if the control for the dependent source is (a) $0.8i_x$; (b) $0.8i_y$. In each case, demonstrate that the absorbed power quantities sum to zero.




■ **FIGURE 3.68**



Problema 3.36 página 69

Find i_x in the circuit of Fig. 3.69.

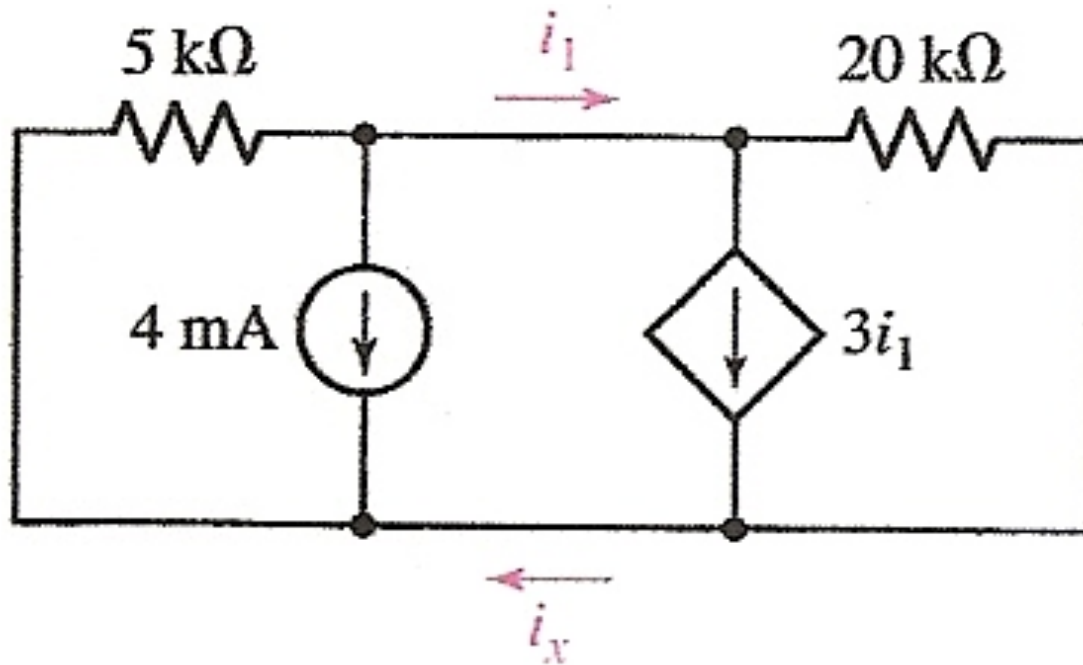


■ **FIGURE 3.69**



Problema 3.37 página 69

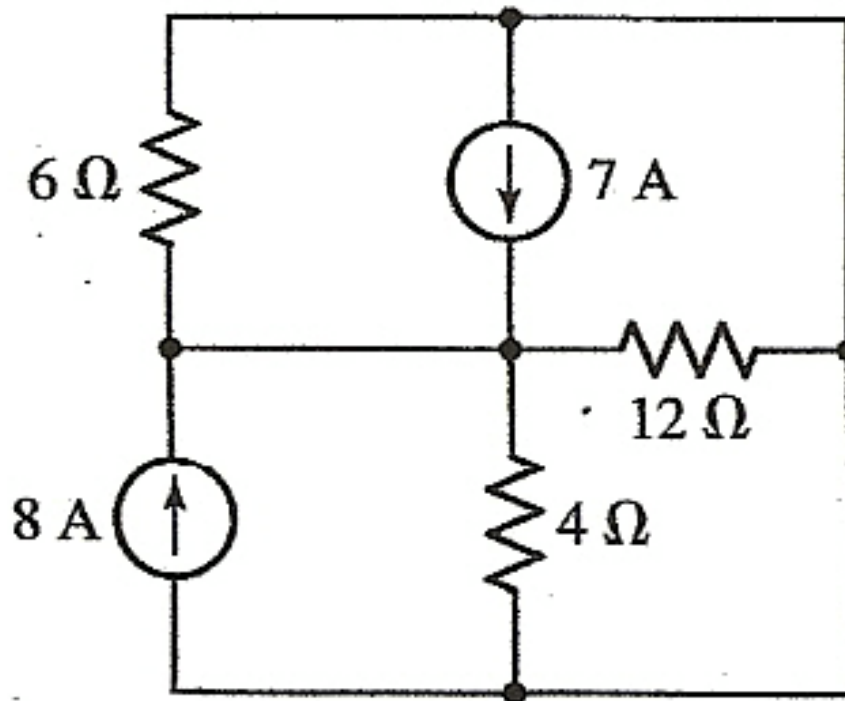
37. Find the power absorbed by each element in the single-node-pair circuit of Fig. 3.70, and show that the sum is equal to zero.



■ **FIGURE 3.70**




Problema 3.58 página 73

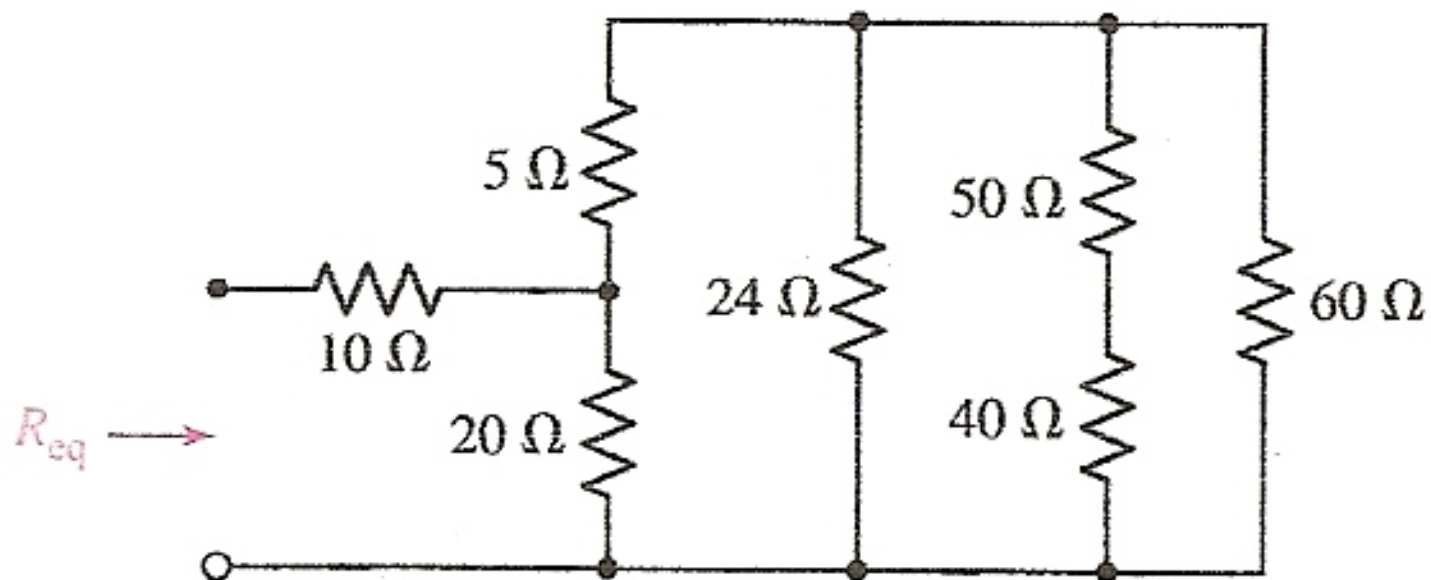

(b)



Problema 3.58 página 73

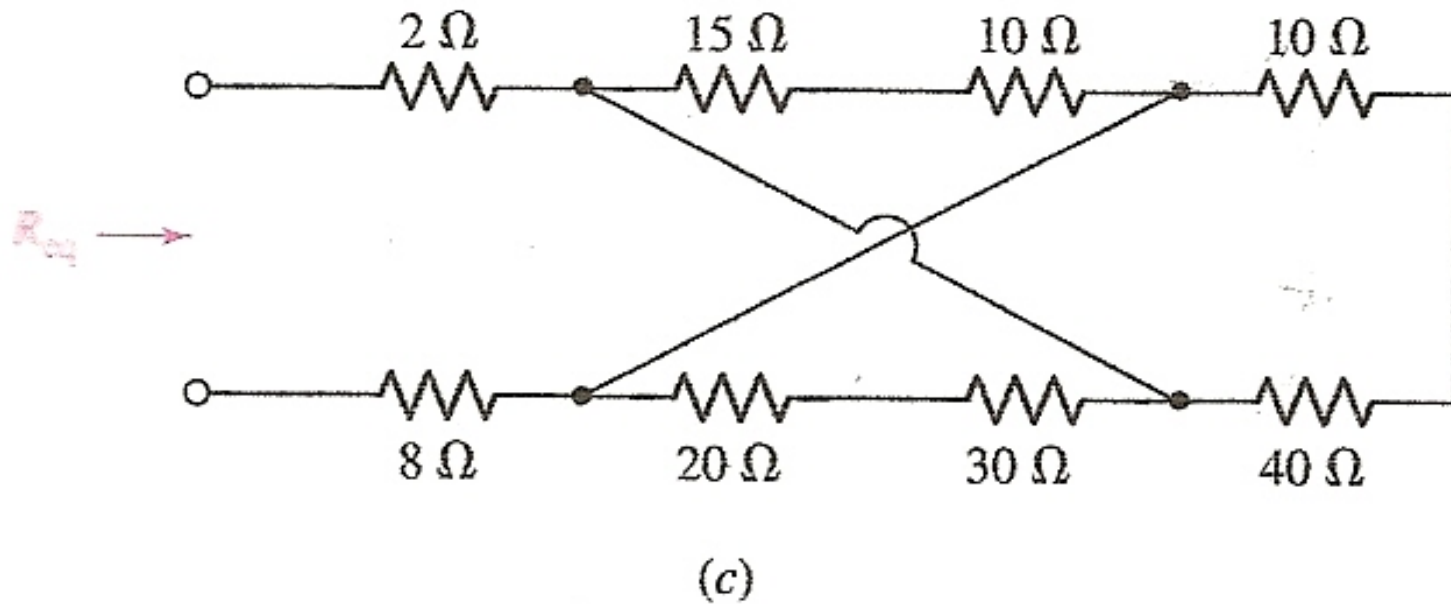

■ **FIGURE 3.89**

Problema 3.64, página 64

64. Use both resistance and source combinations, as well as current division, in the circuit of Fig. 3.94 to find the power absorbed by the $1\ \Omega$, $10\ \Omega$, and $13\ \Omega$ resistors.


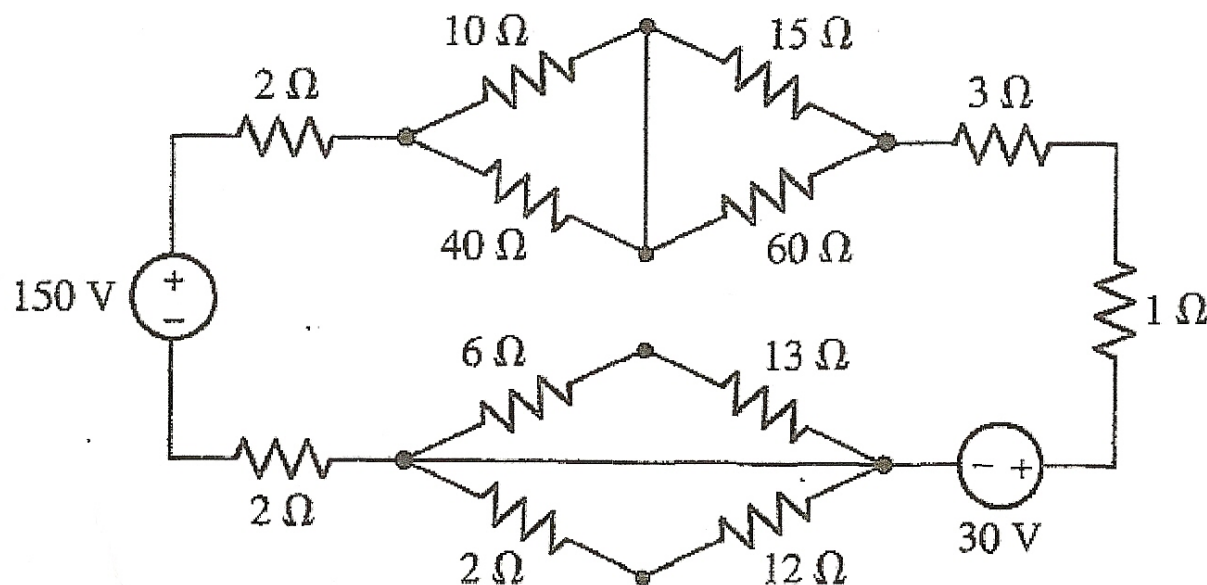



FIGURE 3.94

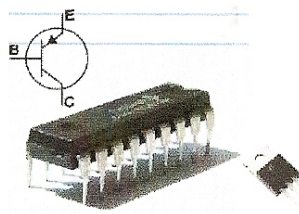



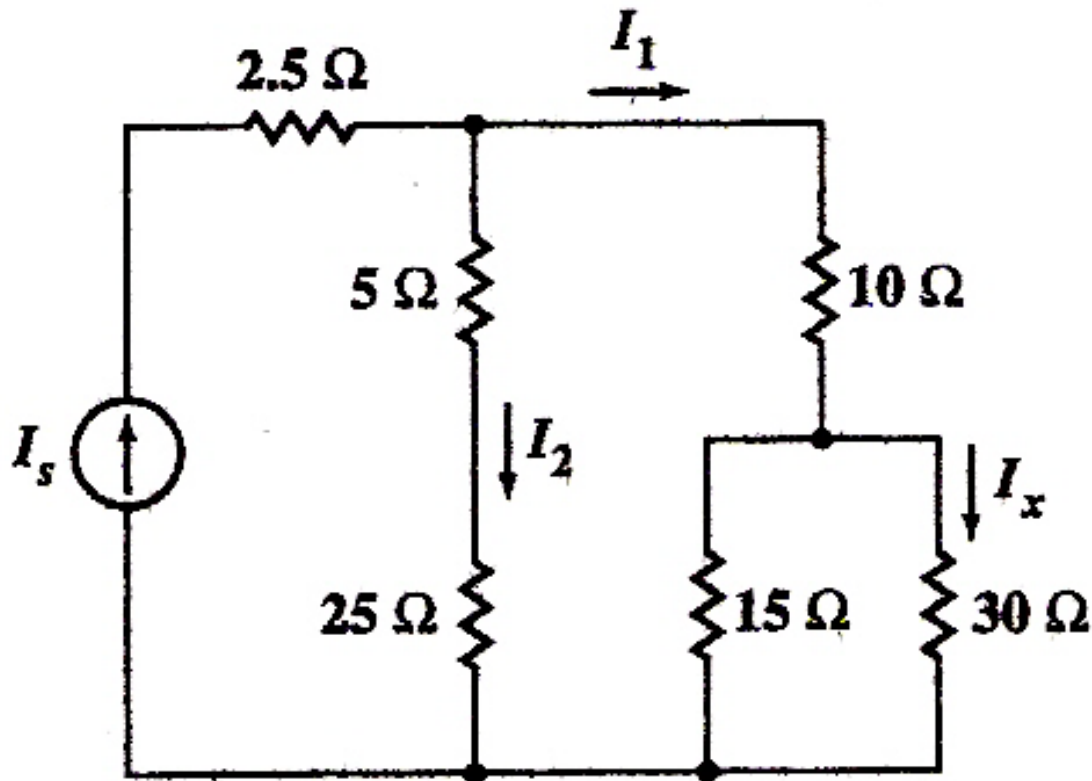Problema 3.82 página 78

Para el circuito de la figura P3 determine la corriente i_x si $I_S = 60$ mA y la potencia que entrega la fuente I_S .



Para el circuito de la figura determine la corriente i_o y la potencia que entrega la fuente de 240 V.

